



# **EENG 5342 Project**

## **Single-Cycle MIPS Processor**

**Anish Goyal and Killian McCrary**

Department of Electrical/Computer Engineering  
Georgia Southern University  
Statesboro, GA

December 3, 2025



# Outline

## 1. Introduction

- 1.1. Motivation
- 1.2. Abstract
- 1.3. What was planned

## 2. Methodology

- 2.1. Design

## 3. Implementation

- 3.1. Block Diagram
- 3.2. Opcode Implementation
- 3.3. Key Components

## 4. Results

- 4.1. Sample Waveform

## 5. Challenges and Improvements

- 5.1. Problems During Design
- 5.2. Potential Improvements
- 5.3. Conclusion

# Introduction

*An overview of the task at hand and what we planned to accomplish.*

# Motivation

Why we chose this project

- Gain hands-on experience with processor architecture
- Understand the datapath and control unit interaction
- Apply VHDL skills to a complex, multi-component system
- Bridge the gap between theoretical CPU design and practical implementation

# Motivation

Why we chose this project

- Gain hands-on experience with processor architecture
- Understand the datapath and control unit interaction
- Apply VHDL skills to a complex, multi-component system
- Bridge the gap between theoretical CPU design and practical implementation

# Motivation

Why we chose this project

- Gain hands-on experience with processor architecture
- Understand the datapath and control unit interaction
- Apply VHDL skills to a complex, multi-component system
- Bridge the gap between theoretical CPU design and practical implementation

# Motivation

Why we chose this project

- Gain hands-on experience with processor architecture
- Understand the datapath and control unit interaction
- Apply VHDL skills to a complex, multi-component system
- Bridge the gap between theoretical CPU design and practical implementation

# Abstract

## Overview of the project and its goals

- Implemented a single-cycle MIPS processor in VHDL
- Supports R-type, I-type, and memory instructions
- Key components include:
  - Program Counter (PC)
  - Instruction Memory
  - Register File (32 registers)
  - ALU with controller
  - Data Memory
  - Main Control Unit
- Validated via functional simulation in Questa/ModelSim



# Abstract

## Overview of the project and its goals

- Implemented a single-cycle MIPS processor in VHDL
- Supports R-type, I-type, and memory instructions
- Key components include:
  - Program Counter (PC)
  - Instruction Memory
  - Register File (32 registers)
  - ALU with controller
  - Data Memory
  - Main Control Unit
- Validated via functional simulation in Questa/ModelSim

# Abstract

## Overview of the project and its goals

- Implemented a single-cycle MIPS processor in VHDL
- Supports R-type, I-type, and memory instructions
- Key components include:
  - Program Counter (PC)
  - Instruction Memory
  - Register File (32 registers)
  - ALU with controller
  - Data Memory
  - Main Control Unit
- Validated via functional simulation in Questa/ModelSim



# Abstract

## Overview of the project and its goals

- Implemented a single-cycle MIPS processor in VHDL
- Supports R-type, I-type, and memory instructions
- Key components include:
  - Program Counter (PC)
  - Instruction Memory
  - Register File (32 registers)
  - ALU with controller
  - Data Memory
  - Main Control Unit
- Validated via functional simulation in Questa/ModelSim

# What was planned

## Our objectives

- Create a fully functional single-cycle MIPS datapath
- Support the following instruction types:
  - R-type: add, sub, and, or, slt
  - I-type: lw, sw
- Integrate all components via schematic capture in Quartus
- Verify correctness through waveform simulation

# What was planned

## Our objectives

- Create a fully functional single-cycle MIPS datapath
- Support the following instruction types:
  - R-type: add, sub, and, or, slt
  - I-type: lw, sw
- Integrate all components via schematic capture in Quartus
- Verify correctness through waveform simulation

# What was planned

## Our objectives

- Create a fully functional single-cycle MIPS datapath
- Support the following instruction types:
  - R-type: add, sub, and, or, slt
  - I-type: lw, sw
- Integrate all components via schematic capture in Quartus
- Verify correctness through waveform simulation

# What was planned

## Our objectives

- Create a fully functional single-cycle MIPS datapath
- Support the following instruction types:
  - R-type: add, sub, and, or, slt
  - I-type: lw, sw
- Integrate all components via schematic capture in Quartus
- Verify correctness through waveform simulation

# What was planned

## Our objectives

- Create a fully functional single-cycle MIPS datapath
- Support the following instruction types:
  - R-type: add, sub, and, or, slt
  - I-type: lw, sw
- Integrate all components via schematic capture in Quartus
- Verify correctness through waveform simulation

# What was planned

## Our objectives

- Create a fully functional single-cycle MIPS datapath
- Support the following instruction types:
  - R-type: add, sub, and, or, slt
  - I-type: lw, sw
- Integrate all components via schematic capture in Quartus
- Verify correctness through waveform simulation

# Methodology

*Detailed explanation of the approach and techniques used.*



# Design

## Overview of the design process

- Based on the classic MIPS single-cycle architecture
- Each instruction executes in one clock cycle
- Datapath connects:
  - PC → Instruction Memory → Register File
  - ALU performs computation
  - Data Memory for load/store operations
- Control signals generated by Main Control and ALU Controller

# Design

## Overview of the design process

- Based on the classic MIPS single-cycle architecture
- Each instruction executes in one clock cycle
- Datapath connects:
  - PC → Instruction Memory → Register File
  - ALU performs computation
  - Data Memory for load/store operations
- Control signals generated by Main Control and ALU Controller

# Design

## Overview of the design process

- Based on the classic MIPS single-cycle architecture
- Each instruction executes in one clock cycle
- Datapath connects:
  - PC → Instruction Memory → Register File
  - ALU performs computation
  - Data Memory for load/store operations
- Control signals generated by Main Control and ALU Controller

# Design

## Overview of the design process

- Based on the classic MIPS single-cycle architecture
- Each instruction executes in one clock cycle
- Datapath connects:
  - PC → Instruction Memory → Register File
  - ALU performs computation
  - Data Memory for load/store operations
- Control signals generated by Main Control and ALU Controller

# Implementation

*Details on how the processor was built and tested.*



# Block Diagram

## Schematic overview of the datapath

- Full datapath designed using Quartus Block Diagram File (.bdf)
- Components instantiated as VHDL symbols
- Wiring completed manually in schematic editor
- Video walkthrough of the block schematic:

<https://youtu.be/19uMkeUoLpE>

# Block Diagram

## Schematic overview of the datapath

- Full datapath designed using Quartus Block Diagram File (.bdf)
- Components instantiated as VHDL symbols
- Wiring completed manually in schematic editor
- Video walkthrough of the block schematic:

<https://youtu.be/19uMkeUoLpE>

# Block Diagram

## Schematic overview of the datapath

- Full datapath designed using Quartus Block Diagram File (.bdf)
- Components instantiated as VHDL symbols
- Wiring completed manually in schematic editor
- Video walkthrough of the block schematic:

<https://youtu.be/19uMkeUoLpE>

# Block Diagram

## Schematic overview of the datapath

- Full datapath designed using Quartus Block Diagram File (.bdf)
- Components instantiated as VHDL symbols
- Wiring completed manually in schematic editor
- Video walkthrough of the block schematic:

<https://youtu.be/19uMkeUoLpE>

# Opcode Implementation

Control signal generation based on instruction opcode

- Main Control decodes 6-bit opcode
- Generates control signals:
  - ALUOp (6-bit)
  - ALUOp[5:4] = ALUOp[5:4] (6-bit)
  - ALUOp[3:2] = ALUOp[3:2] (6-bit)
  - ALUOp[1:0] = ALUOp[1:0] (6-bit)
  - ALUOp[5:4] = ALUOp[5:4] (6-bit)
  - ALUOp[3:2] = ALUOp[3:2] (6-bit)
  - ALUOp[1:0] = ALUOp[1:0] (6-bit)
- ALU Controller uses ALUOp and funct field

Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

Figure: Opcode table for control signal generation

# Opcode Implementation

Control signal generation based on instruction opcode

- Main Control decodes 6-bit opcode
- Generates control signals:
  - RegDst, ALUSrc
  - MemtoReg, RegWrite
  - MemRead, MemWrite
  - Branch, ALUOp
- ALU Controller uses ALUOp and funct field

Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

Figure: Opcode table for control signal generation

# Opcode Implementation

Control signal generation based on instruction opcode

- Main Control decodes 6-bit opcode
- Generates control signals:
  - RegDst, ALUSrc
  - MemtoReg, RegWrite
  - MemRead, MemWrite
  - Branch, ALUOp
- ALU Controller uses ALUOp and funct field

Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

Figure: Opcode table for control signal generation

# Opcode Implementation

Control signal generation based on instruction opcode

- Main Control decodes 6-bit opcode
- Generates control signals:
  - RegDst, ALUSrc
  - MemtoReg, RegWrite
  - MemRead, MemWrite
  - Branch, ALUOp
- ALU Controller uses ALUOp and funct field

Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

Figure: Opcode table for control signal generation

# Opcode Implementation

Control signal generation based on instruction opcode

- Main Control decodes 6-bit opcode
- Generates control signals:
  - RegDst, ALUSrc
  - MemtoReg, RegWrite
  - MemRead, MemWrite
  - Branch, ALUOp
- ALU Controller uses ALUOp and funct field

Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

Figure: Opcode table for control signal generation

# Key Components

Two important components of the datapath

## ALU Controller

- Receives ALUOp from Main Control
- Decodes funct field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register \$0 hardwired to zero

# Key Components

Two important components of the datapath

## ALU Controller

- Receives `ALUOp` from Main Control
- Decodes `funct` field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register `$0` hardwired to zero



# Key Components

Two important components of the datapath

## ALU Controller

- Receives `ALUOp` from Main Control
- Decodes `funct` field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register `$0` hardwired to zero

# Key Components

Two important components of the datapath

## ALU Controller

- Receives `ALUOp` from Main Control
- Decodes `funct` field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register \$0 hardwired to zero

# Key Components

Two important components of the datapath

## ALU Controller

- Receives `ALUOp` from Main Control
- Decodes `funct` field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register \$0 hardwired to zero

# Key Components

Two important components of the datapath

## ALU Controller

- Receives `ALUOp` from Main Control
- Decodes `funct` field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register \$0 hardwired to zero

# Key Components

Two important components of the datapath

## ALU Controller

- Receives `ALUOp` from Main Control
- Decodes `funct` field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register `$0` hardwired to zero

# Key Components

Two important components of the datapath

## ALU Controller

- Receives `ALUOp` from Main Control
- Decodes `funct` field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register `$0` hardwired to zero

# Key Components

Two important components of the datapath

## ALU Controller

- Receives `ALUOp` from Main Control
- Decodes `funct` field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register `$0` hardwired to zero



# Key Components

Two important components of the datapath

## ALU Controller

- Receives `ALUOp` from Main Control
- Decodes `funct` field for R-type
- Outputs 4-bit ALU control signal
- Supports: ADD, SUB, AND, OR, SLT

## Register File

- 32 general-purpose registers
- Dual read ports, single write port
- Synchronous write on clock edge
- Register `$0` hardwired to zero

# Results

*Summary of simulation results.*

# Sample Waveform

Functional simulation output

## Initial Conditions:

- Registers \$0 – \$31 initialized to values 0 – 31

## Test Instructions:

```
x"012a4020"  -- 0x012A4020 -> add $8, $9, $10
x"01285022"  -- 0x01285022 -> sub $10, $9, $8
x"8e510000"  -- 0x8E510000 -> lw $17, 0($18)
x"ae290004"  -- 0xAE290004 -> sw $9, 4($17)
```

# Sample Waveform

## Simulation results

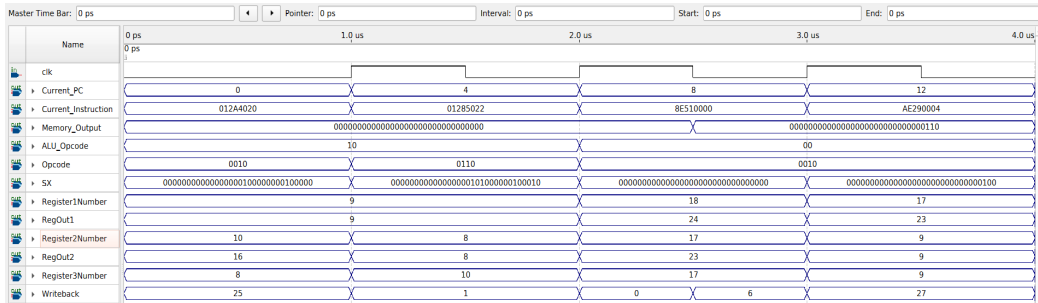


Figure: Waveform output from Questa/ModelSim functional simulation

# Challenges and Improvements

*Challenges encountered and potential future work.*

# Problems During Design

Issues encountered during implementation

- **Bus naming convention** – inconsistent naming caused wiring issues
- Quartus schematic editor – unreliable click registration and net changes
- Input/output pin naming – required careful matching
- Constant value generation – needed explicit constant blocks
- Functional simulation – required `voptargs="+acc"` on personal laptop

# Problems During Design

Issues encountered during implementation

- **Bus naming convention** – inconsistent naming caused wiring issues
- **Quartus schematic editor** – unreliable click registration and net changes
- **Input/output pin naming** – required careful matching
- **Constant value generation** – needed explicit constant blocks
- **Functional simulation** – required `voptargs="+acc"` on personal laptop

# Problems During Design

Issues encountered during implementation

- **Bus naming convention** – inconsistent naming caused wiring issues
- **Quartus schematic editor** – unreliable click registration and net changes
- **Input/output pin naming** – required careful matching
- **Constant value generation** – needed explicit constant blocks
- **Functional simulation** – required `voptargs="+acc"` on personal laptop



# Problems During Design

Issues encountered during implementation

- **Bus naming convention** – inconsistent naming caused wiring issues
- **Quartus schematic editor** – unreliable click registration and net changes
- **Input/output pin naming** – required careful matching
- **Constant value generation** – needed explicit constant blocks
- **Functional simulation** – required `voptargs="+acc"` on personal laptop

# Problems During Design

Issues encountered during implementation

- **Bus naming convention** – inconsistent naming caused wiring issues
- **Quartus schematic editor** – unreliable click registration and net changes
- **Input/output pin naming** – required careful matching
- **Constant value generation** – needed explicit constant blocks
- **Functional simulation** – required `voptargs="+acc"` on personal laptop

# Problems During Design

## Additional issues

- **XOR overriding SUB** – class code had XOR opcode conflicting with SUB; required control value changes
- **Questa license server** – needed to set SALT\_LICENSE\_SERVER environment variable
- **MemToReg mux polarity** – flipped polarity inherent in reference diagram
- **5-bit 2-to-1 mux** – needed to create a special 5-bit mux before register file

# Problems During Design

## Additional issues

- **XOR overriding SUB** – class code had XOR opcode conflicting with SUB; required control value changes
- **Questa license server** – needed to set SALT\_LICENSE\_SERVER environment variable
- **MemToReg mux polarity** – flipped polarity inherent in reference diagram
- **5-bit 2-to-1 mux** – needed to create a special 5-bit mux before register file

# Problems During Design

## Additional issues

- **XOR overriding SUB** – class code had XOR opcode conflicting with SUB; required control value changes
- **Questa license server** – needed to set SALT\_LICENSE\_SERVER environment variable
- **MemToReg mux polarity** – flipped polarity inherent in reference diagram
- **5-bit 2-to-1 mux** – needed to create a special 5-bit mux before register file

# Problems During Design

## Additional issues

- **XOR overriding SUB** – class code had XOR opcode conflicting with SUB; required control value changes
- **Questa license server** – needed to set SALT\_LICENSE\_SERVER environment variable
- **MemToReg mux polarity** – flipped polarity inherent in reference diagram
- **5-bit 2-to-1 mux** – needed to create a special 5-bit mux before register file

# Potential Improvements

## Future work and extensions

- **Half-period asymmetry** – add half cycle of zero before first rising edge
- **Pipelining** – implement 5-stage pipeline with data hazard detection
- **Jump support** – add unconditional jump (j) instruction
- **Real-time output** – display register/memory values to console
- **Live instruction input** – avoid recompilation for instruction changes

# Potential Improvements

## Future work and extensions

- **Half-period asymmetry** – add half cycle of zero before first rising edge
- **Pipelining** – implement 5-stage pipeline with data hazard detection
- **Jump support** – add unconditional jump (j) instruction
- **Real-time output** – display register/memory values to console
- **Live instruction input** – avoid recompilation for instruction changes



# Potential Improvements

## Future work and extensions

- **Half-period asymmetry** – add half cycle of zero before first rising edge
- **Pipelining** – implement 5-stage pipeline with data hazard detection
- **Jump support** – add unconditional jump (j) instruction
- **Real-time output** – display register/memory values to console
- **Live instruction input** – avoid recompilation for instruction changes

# Potential Improvements

## Future work and extensions

- **Half-period asymmetry** – add half cycle of zero before first rising edge
- **Pipelining** – implement 5-stage pipeline with data hazard detection
- **Jump support** – add unconditional jump (j) instruction
- **Real-time output** – display register/memory values to console
- **Live instruction input** – avoid recompilation for instruction changes

# Potential Improvements

## Future work and extensions

- **Half-period asymmetry** – add half cycle of zero before first rising edge
- **Pipelining** – implement 5-stage pipeline with data hazard detection
- **Jump support** – add unconditional jump (j) instruction
- **Real-time output** – display register/memory values to console
- **Live instruction input** – avoid recompilation for instruction changes

# Potential Improvements

## Additional enhancements

- **Pipeline registers** – add registers between stages
- **Additional operations** – multiplication, division, shifting
- **Data forwarding** – bypass paths for hazard mitigation
- **FPGA deployment** – synthesize and run on actual hardware

# Potential Improvements

## Additional enhancements

- **Pipeline registers** – add registers between stages
- **Additional operations** – multiplication, division, shifting
- **Data forwarding** – bypass paths for hazard mitigation
- **FPGA deployment** – synthesize and run on actual hardware

# Potential Improvements

## Additional enhancements

- **Pipeline registers** – add registers between stages
- **Additional operations** – multiplication, division, shifting
- **Data forwarding** – bypass paths for hazard mitigation
- **FPGA deployment** – synthesize and run on actual hardware

# Potential Improvements

## Additional enhancements

- **Pipeline registers** – add registers between stages
- **Additional operations** – multiplication, division, shifting
- **Data forwarding** – bypass paths for hazard mitigation
- **FPGA deployment** – synthesize and run on actual hardware

# Conclusion

## Summary of results

- Successfully implemented a single-cycle MIPS processor
- Supports R-type (add, sub) and I-type (lw, sw) instructions
- Verified functionality through waveform simulation
- Gained practical experience with datapath design and control logic
- Identified areas for future improvement and extension



# Conclusion

## Summary of results

- Successfully implemented a single-cycle MIPS processor
- Supports R-type (add, sub) and I-type (lw, sw) instructions
- Verified functionality through waveform simulation
- Gained practical experience with datapath design and control logic
- Identified areas for future improvement and extension

# Conclusion

## Summary of results

- Successfully implemented a single-cycle MIPS processor
- Supports R-type (add, sub) and I-type (lw, sw) instructions
- Verified functionality through waveform simulation
- Gained practical experience with datapath design and control logic
- Identified areas for future improvement and extension

# Conclusion

## Summary of results

- Successfully implemented a single-cycle MIPS processor
- Supports R-type (add, sub) and I-type (lw, sw) instructions
- Verified functionality through waveform simulation
- Gained practical experience with datapath design and control logic
- Identified areas for future improvement and extension

# Conclusion

## Summary of results

- Successfully implemented a single-cycle MIPS processor
- Supports R-type (add, sub) and I-type (lw, sw) instructions
- Verified functionality through waveform simulation
- Gained practical experience with datapath design and control logic
- Identified areas for future improvement and extension

## References

- [1] M. Ahad, EENG 5342 lecture notes. Aug. 2025.
- [2] D. A. Patterson and J. L. Hennessy, *Computer organization and design: The hardware/software interface (MIPS edition)*, 6th Edition. Morgan Kaufmann, 2020.



# **EENG 5342 Project**

## **Single-Cycle MIPS Processor**

*Thank you for your attention!*

**Anish Goyal and Killian McCrary**

Department of Electrical/Computer Engineering  
Georgia Southern University  
Statesboro, GA

December 3, 2025

